

Esercizio 1 – una possibile soluzione

La tabella di figura contiene un ciclo di tre stati. È pertanto necessario inserire uno stato ponte. Ad esempio, codificando gli stati come $S0=00$, $S1=01$, $S2=10$, è possibile usare $S0$ come stato ponte nelle transizioni $S1-S2$. La tabella modificata è la seguente (si notino le celle in grassetto):

x_1x_0	00	01	11	10	z_1z_0
s_0	--	S1	S0	S2	11
s_1	S1	S1	S0	S0	01
s_2	S2	S0	S0	S2	10

x_1x_0	00	01	11	10	z_1z_0
y_1y_0	00	01	11	10	11
01	01	01	00	00	01
11	--	--	--	--	--
10	10	00	00	10	10

a_1a_0

tabella di applicazione
del latch SR

q	q'	s	r
0	0	0	-
0	1	1	0
1	0	0	1
1	1	-	0

x_1x_0	00	01	11	10
y_1y_0	00	0-	0-	10
01	0-	0-	0-	0-
11	--	--	--	--
10	-0	01	01	-0

S_1r_1

x_1x_0	00	01	11	10
y_1y_0	00	10	0-	0-
01	-0	-0	01	01
11	--	--	--	--
10	0-	0-	0-	0-

S_0r_0


$$\overline{s_1} = x_0 + y_0 \rightarrow s_1 = \overline{x_0 + y_0}$$

$$\overline{r_1} = x_0 \rightarrow r_1 = x_0$$

$$\overline{s_0} = x_1 + y_1 \rightarrow s_0 = \overline{x_1 + y_1}$$

$$\overline{r_0} = x_1 \rightarrow r_0 = x_1$$

Per quanto riguarda le uscite, si ha: $z_0 = \overline{y_1}$, $z_1 = \overline{y_0}$

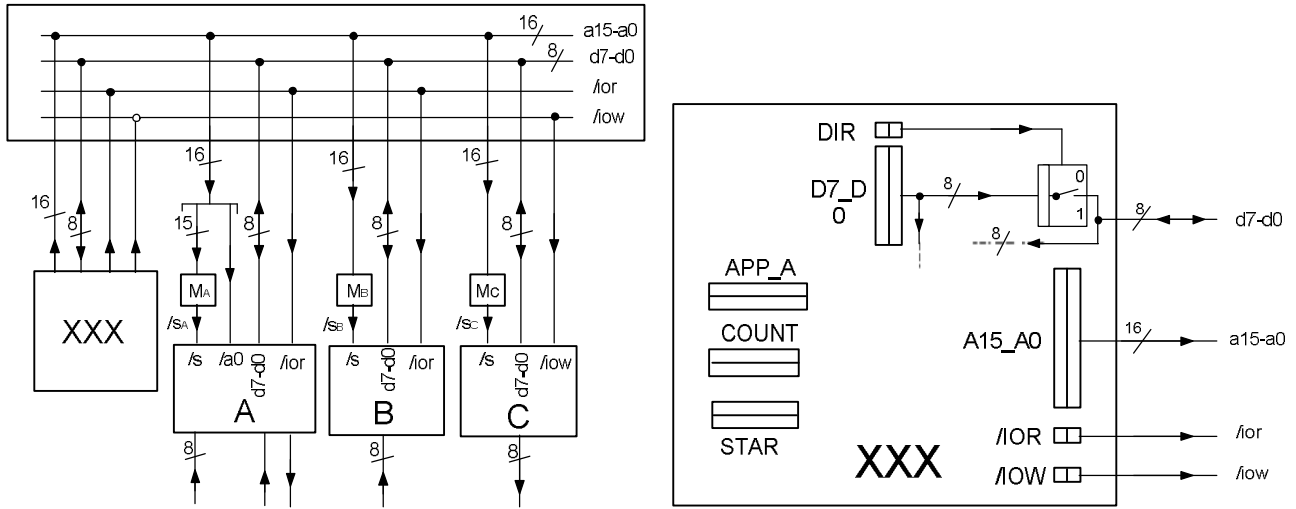Esercizio 2 - una possibile soluzione:

```

wire sA_=(a15_a0=='H0100')|(a15_a0=='H0101')?0:1;
wire sB_=(a15_a0=='H0120')?0:1;
wire sC_=(a15_a0=='H0140')?0:1;

```

```

module XXX(d7_d0, a15_a0, ior_, iow_, clock, reset_);
input      clock, reset_;
inout  [7:0] d7_d0;
output [15:0] a15_a0;
output      ior_, iow_;

reg        IOR_, IOW_; assign ior_=IOR_; assign iow_=IOW_;
reg        DIR;
reg [15:0] A15_A0;   assign a15_a0=A15_A0;
reg [7:0]  D7_D0;    assign d7_d0 =(DIR==1)?D7_D0:'HZZ; //FORCHETTA
reg [7:0]  APP_A;
reg [6:0]  COUNT;
reg [3:0]  STAR;
parameter S0=0,S1=1,S2=2,S3=3,S4=4,S5=5,S6=6,S7=7,S8=8,S9=9,S10=10,S11=11;
parameter Num_Periodi=100;
always @(reset_==0) begin APP_A<='H00; DIR<=0; COUNT<=Num_Periodi;
                          IOR_<=1; IOW_<=1; STAR<=S0; end
always @(posedge clock) if (reset_==1) #3
  casex(STAR)
    S0: begin COUNT<=COUNT-1; A15_A0<='H0120; STAR<=S1; end
    S1: begin COUNT<=COUNT-1; IOR_<=0; STAR<=S2; end
    S2: begin COUNT<=COUNT-1; D7_D0<=d7_d0+APP_A; IOR_<=1; A15_A0<='H0140;
          DIR<=1; STAR<=S3; end
    S3: begin COUNT<=COUNT-1; IOW_<=0; STAR<=S4; end
    S4: begin COUNT<=COUNT-1; IOW_<=1; STAR<=S5; end
    S5: begin COUNT<=COUNT-1; DIR<=0; A15_A0<='H0100; STAR<=S6; end
    S6: begin COUNT<=COUNT-1; IOR_<=0; STAR<=S7; end
    S7: begin COUNT<=COUNT-1; IOR_<=1; STAR<=(d7_d0[0]==0)?S6:S8; end
    S8: begin COUNT<=COUNT-1; A15_A0<='H0101; STAR<=S9; end
    S9: begin COUNT<=COUNT-1; IOR_<=0; STAR<=S10; end
    S10: begin COUNT<=COUNT-1; APP_A<=d7_d0; IOR_<=1; STAR<=S11; end
    S11: begin COUNT<=(COUNT==1)?Num_Periodi:COUNT-1;
           STAR<=(COUNT==1)?S0:S11; end
  endcase
endmodule

```