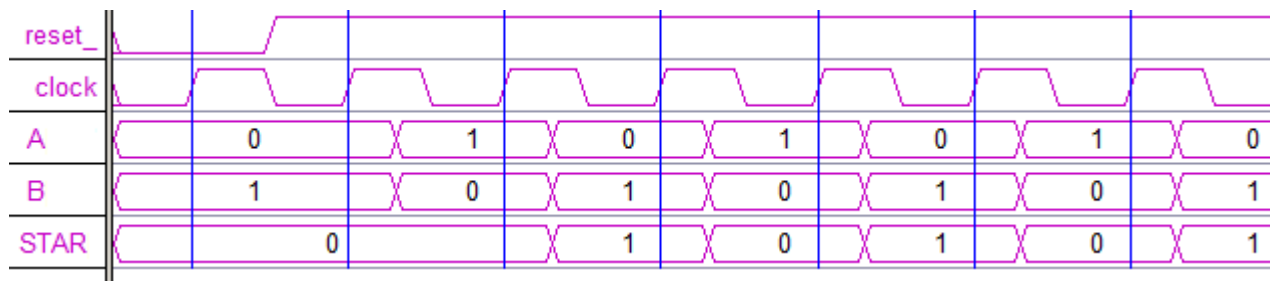


***Per entrare nell'ottica delle temporizzazioni  
delle reti con registri operativi e registro di stato***

```
module XXX(clock,reset_);  
  input          clock, reset_;  
  
  //Registri Operativi  
  reg A,B;  
  
  //Registro di Stato  
  reg STAR;  
  parameter S0=0,S1=1;  
  
  always @(reset_==0) begin A<=0; B<=1; STAR<=S0; end  
  always @(posedge clock)if (reset_==1) #3  
    casex(STAR)  
      S0: begin A<=A+1; B<=A; STAR<=(A==0)?S0:S1; end  
      S1: begin B<=A; A<=B; STAR<=S0; end  
    endcase  
endmodule
```



## ***Descrizioni di un Contatore, modulo 4, delle sequenze in ingresso del tipo 11,01,10***

### **Modello di Mealy Ritardato**

```
module Riconoscitore_e_Contatore_Modulo_4(z1_z0,x1_x0,clock,reset_);
input      clock,reset_;
input  [1:0] x1_x0;
output [1:0] z1_z0;
reg  [1:0] COUNT;    assign z1_z0=COUNT;
reg  [3:0] STAR;
parameter  S0=0,S1=1,S2=2,S3=3,S4=4,S5=5,S6=6,
           S7=7,S8=8,S9=9, S10=10,S11=11;
always @(reset_==0) begin COUNT<=0; STAR<=S0;
always @(posedge clock) if (reset_==1) #3
caseex(STAR)
  S0 : begin COUNT<=0; STAR<=(x1_x0=='B11')?S1:S0; end
  S1 : begin COUNT<=0; STAR<=(x1_x0=='B01')?S2:(x1_x0=='B11')?S1:S0; end
  S2 : begin COUNT<=(x1_x0=='B10')?1:0;
        STAR<=(x1_x0=='B11')?S1:(x1_x0=='B10')?S3:S0; end
  S3 : begin COUNT<=1; STAR<=(x1_x0=='B11')?S4:S3; end
  S4 : begin COUNT<=1; STAR<=(x1_x0=='B01')?S5:(x1_x0=='B11')?S4:S3; end
  S5 : begin COUNT<=(x1_x0=='B10')?2:1;
        STAR<=(x1_x0=='B11')?S4:(x1_x0=='B10')?S6:S3; end
  S6 : begin COUNT<=2; STAR<=(x1_x0=='B11')?S7:S6; end
  S7 : begin COUNT<=2; STAR<=(x1_x0=='B01')?S8:(x1_x0=='B11')?S7:S6; end
  S8 : begin COUNT<=(x1_x0=='B10')?3:2;
        STAR<=(x1_x0=='B11')?S7:(x1_x0=='B10')?S9:S6; end
  S9 : begin COUNT<=3; STAR<=(x1_x0=='B11')?S10:S9; end
  S10: begin COUNT<=3; STAR<=(x1_x0=='B01')?S11:(x1_x0=='B11')?S10:S9; end
  S11: begin COUNT<=(x1_x0=='B10')?0:3;
        STAR<=(x1_x0=='B11')?S10:(x1_x0=='B10')?S0:S9; end
endcase
endmodule
```

### **Modello con Registri Operativi e Registro di Stato**

```
module Riconoscitore_e_Contatore_Modulo_4(z1_z0,x1_x0,clock,reset_);
input      clock,reset_;
input  [1:0] x1_x0;
output [1:0] z1_z0;
//Registro Operativo
reg  [1:0] COUNT;    assign z1_z0=COUNT;
//Registro di Stato
reg  [1:0] STAR;    parameter S0=0,S1=1,S2=2;
always @(reset_==0) begin COUNT<=0; STAR<=S0;
always @(posedge clock) if (reset_==1) #3
caseex(STAR)
  S0: begin COUNT<=COUNT; STAR<=(x1_x0=='B11')?S1:S0; end
  S1: begin COUNT<=COUNT; STAR<=(x1_x0=='B01')?S2:(x1_x0=='B11')?S1:S0; end
  S2: begin COUNT<=(x1_x0=='B10')?(COUNT+1):COUNT;
        STAR<=(x1_x0=='B11')?S1:S0; end
endcase
endmodule
```